

# CHAPTER TWENTY FOUR

---


## *CMOS Combinational Logic Circuits*

# Introduction


---

This chapter presents the structure of multi-input CMOS gates such as NANDs, NORs, AND-OR-Inverts (AOIs)

# CMOS Inverter

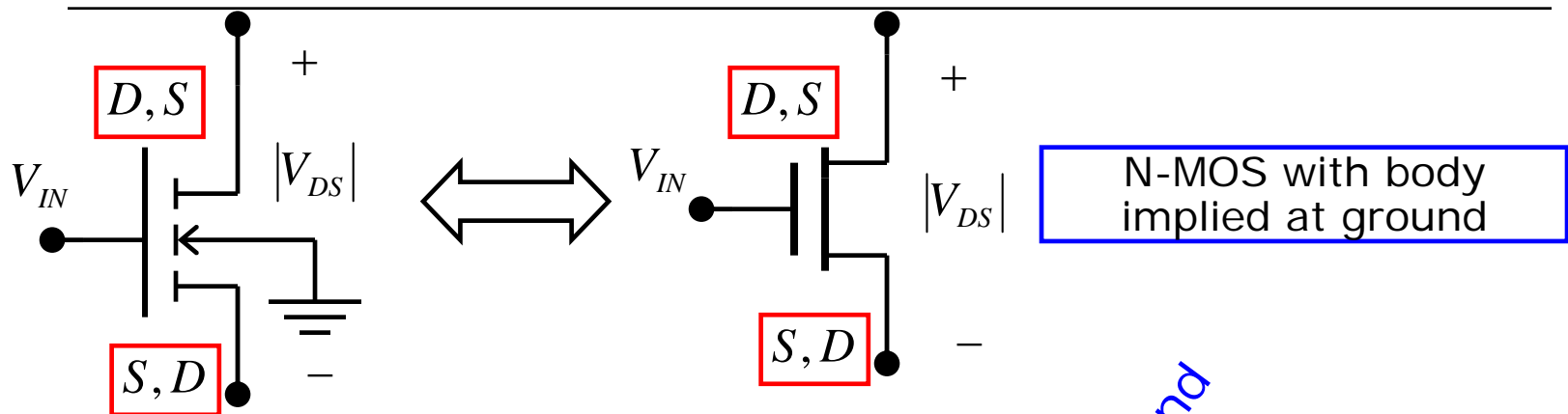

Shorthand symbols

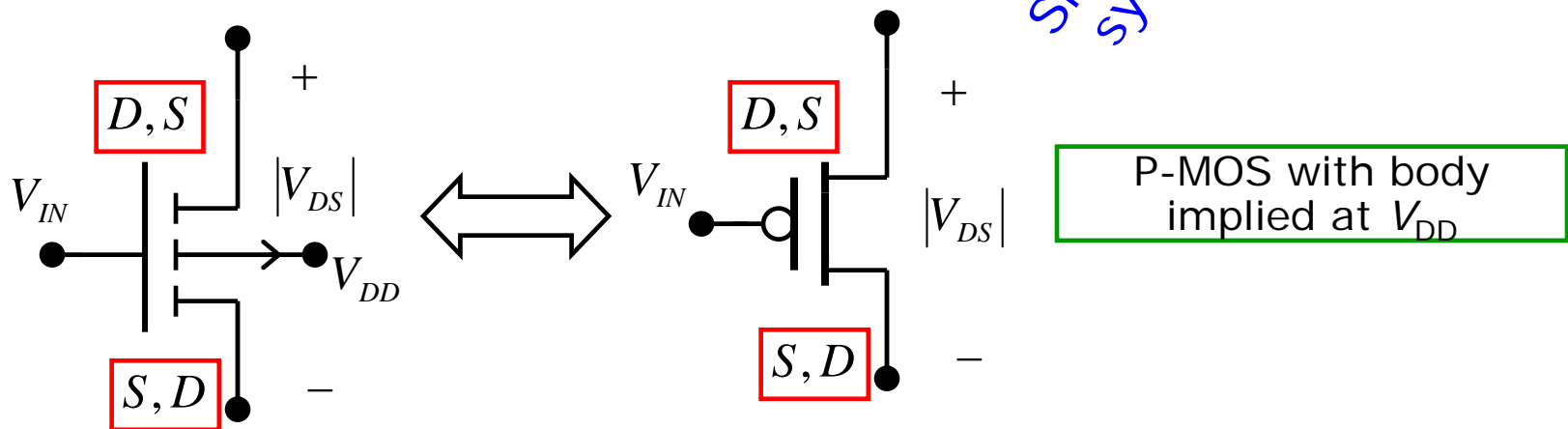

# CMOS Inverter


When  $V_{IN}$  is low, i.e.  $V_{IN} = V_{GS} < V_{TN}$ :

→  $N$  is "off",  $P$  is active "on"

When  $V_{IN}$  is high, i.e.  $V_{IN} = V_{DD} - V_{SG} > V_{TP}$ :

→  $P$  is "off",  $N$  is active "on"


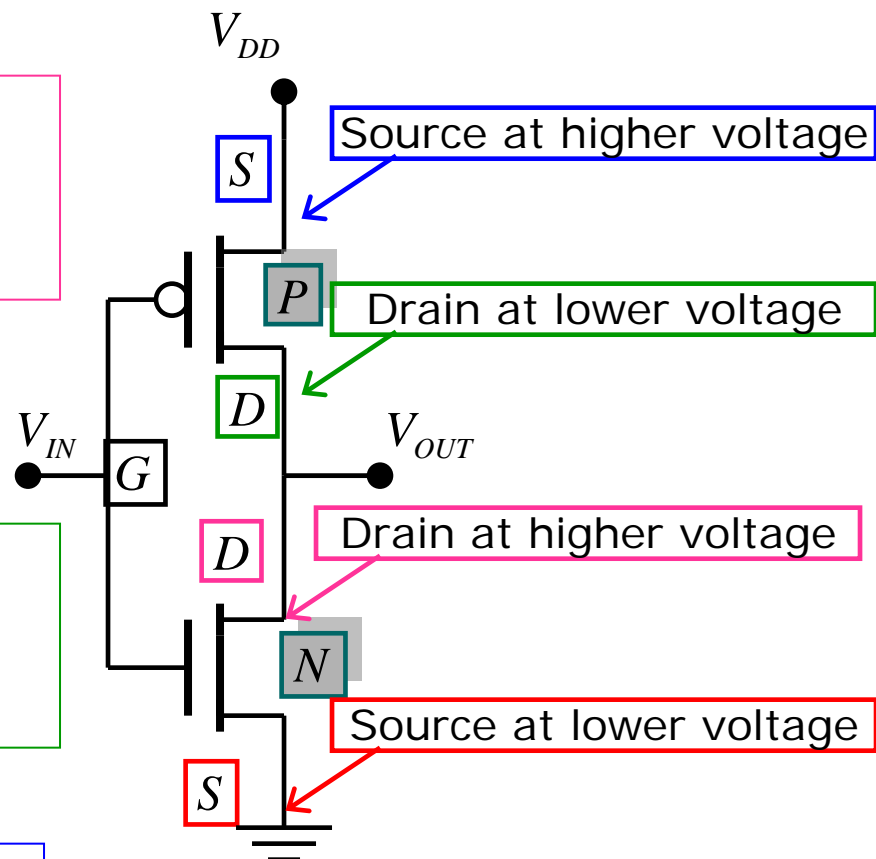
Thus, for input high and low states, both devices never conduct simultaneously



# CMOS NAND Gate

$V_A$	$V_B$	$N_A$	$N_B$	$P_A$	$P_B$	$V_{OUT}$
low	low	off	off	on	on	high
low	high	off	on	on	off	high
high	low	on	off	off	on	high
high	high	on	on	off	off	low



NAND

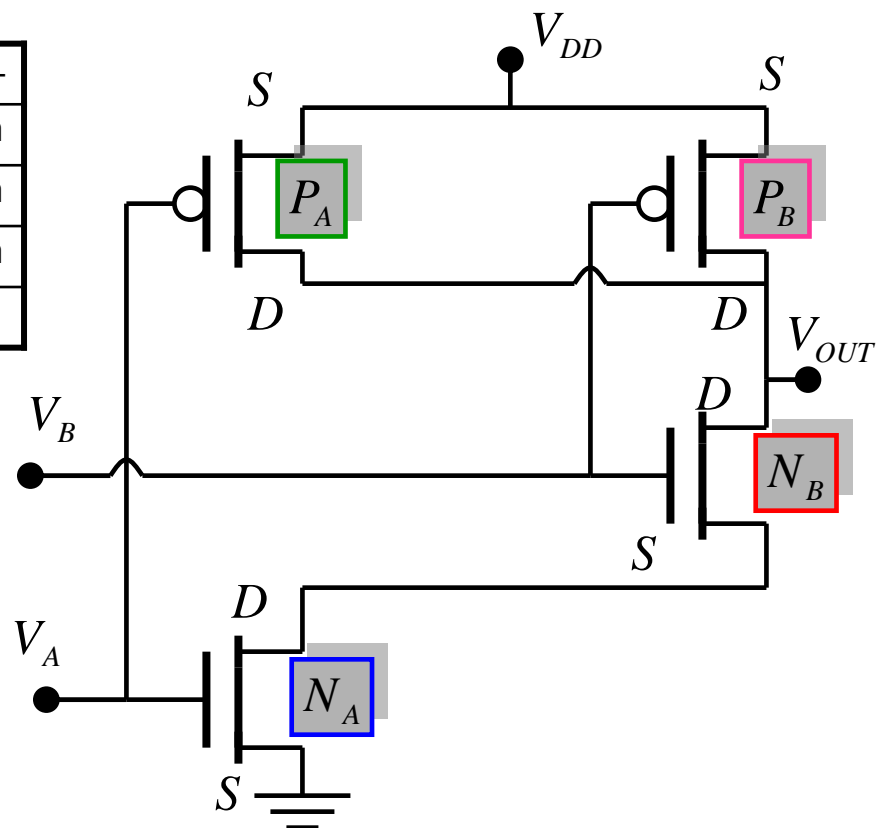 


# CMOS NOR Gate

$V_A$	$V_B$	$N_A$	$N_B$	$P_A$	$P_B$	$V_{OUT}$
low	low	off	off	on	on	high
low	high	off	on	on	off	low
high	low	on	off	off	on	low
high	high	on	on	off	off	low


NOR

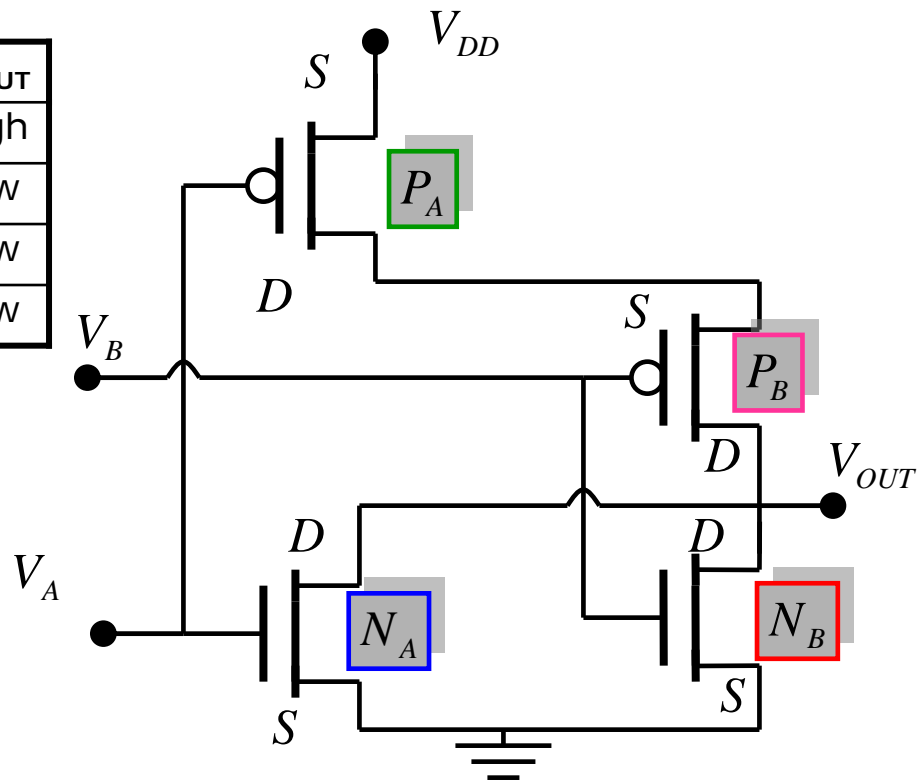 


# CMOS AND Gate

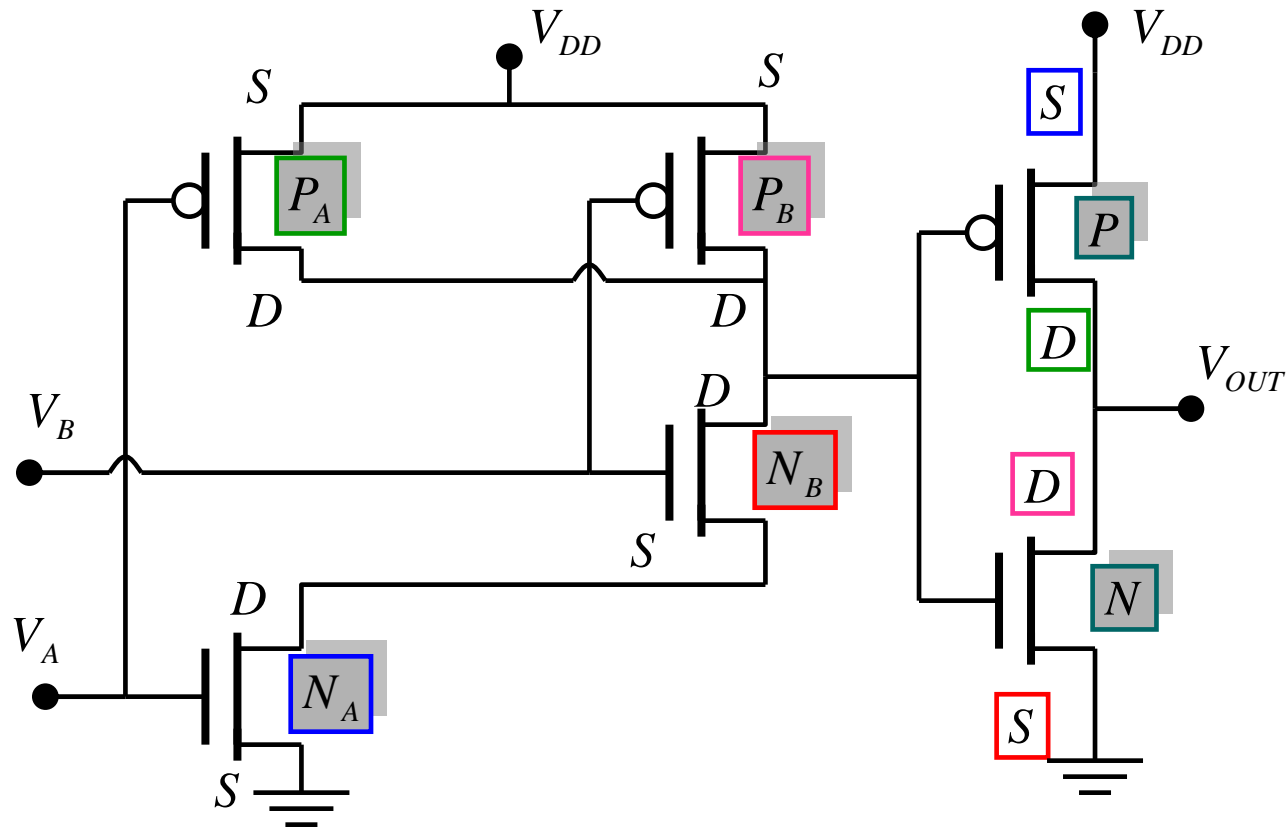

AND

 


# CMOS OR Gate

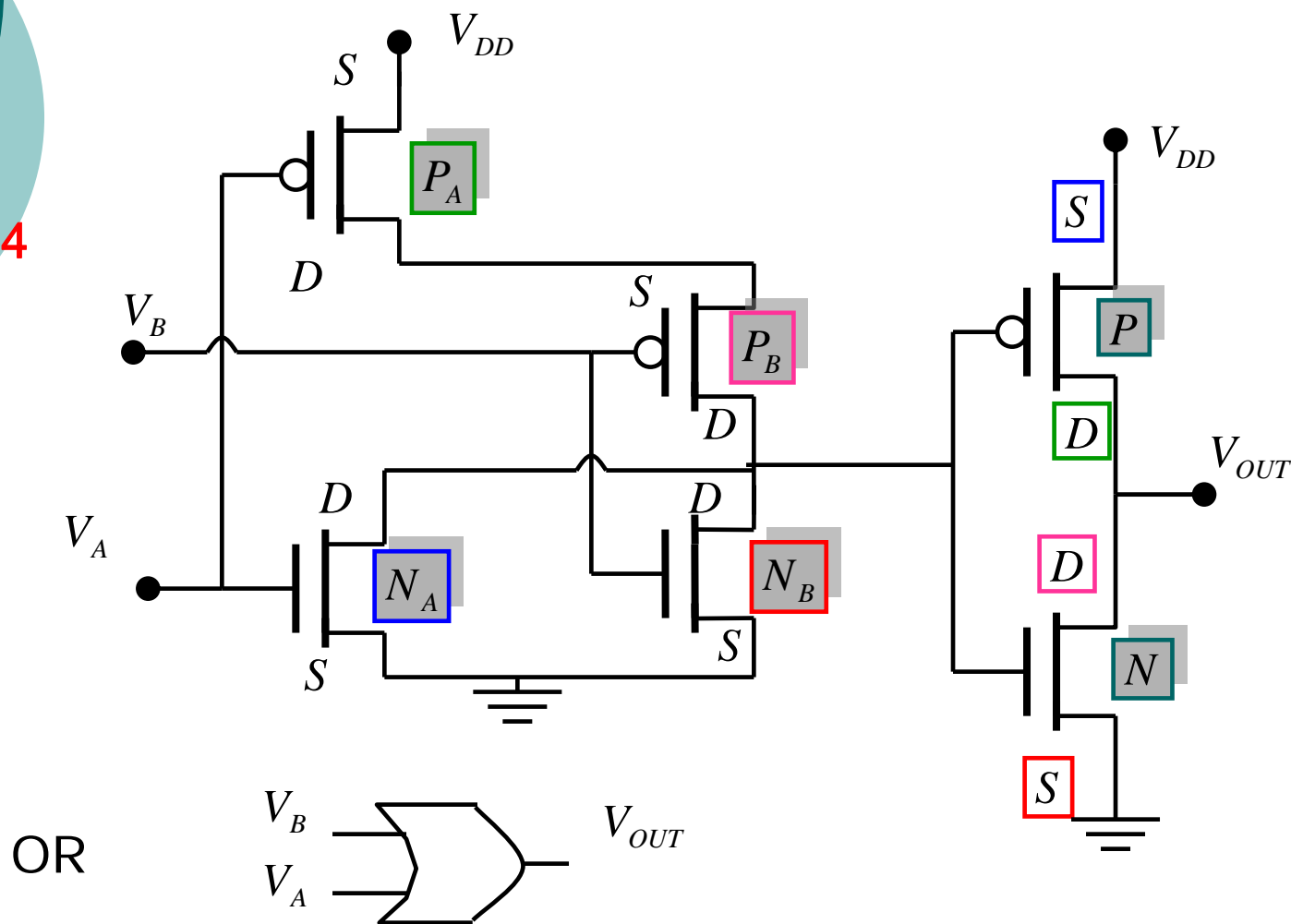




# CMOS AND-OR-Inverter Gate

---

 

# CMOS XOR Gate

---

 

$$F = \overline{A} \bullet A + \overline{A} \bullet B + \overline{B} \bullet A + \overline{B} \bullet B = \overline{A} \bullet B + \overline{B} \bullet A$$

- 
- HW #13: Solve Problems: 24.1-6, 24.25